

Closed Loop (contd)

$$P = \frac{V_1 V_2 D (1-D)}{2 f_{SW} L}$$

Control input: D
Output: V_{out}

↓
small $D / d \rightarrow$ small power

$d = V_1 S \rightarrow$ max power ✓

$d > V_1 S \rightarrow$ decrease power again

Output Capacitor

Energy balance:

$$P_{C-in} - P_{C-out} = P_{C-stored}$$

$$P_{C-in} = \text{Power from DAB} = P$$

$$P_{C-out} = \text{Power consumed by power} = \frac{V_{out}^2}{R_{load}}$$

$$P_{C-stored} = \text{Energy change in Cap / second}$$

$$E = \frac{1}{2} C V_{out}^2 \rightarrow \frac{dE}{dt} = \frac{d}{dt} \left(\frac{1}{2} C V_{out}^2 \right)$$

$$P_{\text{out}(\text{steady})} = \frac{V_1 V_2' D(1-D)}{2 f_{\text{sw}} L} = \frac{V_{\text{out}}^2}{R_{\text{load}}} \quad (3)$$

Add small perturbations

System is slightly disturbed from

Steady state:

$$d = D + \hat{d}$$

$$V_{\text{out}} = V_0 + \hat{v}$$

\hat{d} = small change in phase shift

\hat{v} = small change in output voltage

Substitute (2) with d, V_{out}

$$P_{C-\text{in}} - P_{C-\text{out}} = P_{C-\text{stored}}$$

$$\frac{V_1 V_2' d(1-d)}{2 f_{\text{sw}} L} - \frac{V_{\text{out}}^2}{R_{\text{load}}} = \left(V_{\text{out}} \frac{d V_{\text{out}}}{d \hat{d}} \right)$$

$$\frac{V_1 V_2' (D + \hat{d})(1 - (D + \hat{d}))}{2 f_{\text{sw}} L} - \frac{(V_0 + \hat{v})^2}{R_{\text{load}}} =$$

$$\left((V_0 + \hat{v}) \frac{d(V_0 + \hat{v})}{d \hat{v}} \right)$$

$$(D + \hat{d})(1 - (D + \hat{d})) = (D + \hat{d})(1 - D - \hat{d})$$

$$= (D + \hat{d}) - D(D + \hat{d}) - \hat{d}(D + \hat{d})$$

$$= D + \hat{d} - D^2 - D\hat{d} - D\hat{d} - \hat{d}^2$$

$$= -D^2 - \hat{d}^2 - 2D\hat{d} + D + \hat{d}$$

$$= D(1 - D) + \hat{d}(1 - 2D) - \hat{d}^2$$

\hat{d} = small $\rightarrow \hat{d}^2$ = very small \rightarrow drop \hat{d}^2

$$= D(1 - D) + \hat{d}(1 - 2D)$$

Therefore,

$$P_{C-in} = \frac{V_1 V_2'}{2 f_{sw} L} [D(1 - D) + \hat{d}(1 - 2D)]$$

$$= \frac{V_1 V_2' D(1 - D)}{2 f_{sw} L} + \frac{V_1 V_2' (1 - 2D) \hat{d}}{2 f_{sw} L}$$

$$P_{C-in} = P_{I(steady)} + Gain_P \times \hat{d} \quad (1)$$

$$P_{C-out} = \frac{(V_o + v)^2}{R_{load}},$$

$$(V_0 + \hat{v})^2 = V_0^2 + 2V_0\hat{v} + \hat{v}^2$$

\hat{v}^2 = very small \rightarrow drop \hat{v}^2

$$(V_0 + \hat{v})^2 \approx V_0^2 + 2V_0\hat{v}$$

Therefore,

$$P_{C-out} = \frac{V_0^2 + 2V_0\hat{v}}{R_{load}}$$

$$= \frac{V_0^2}{R_{load}} + \frac{2V_0\hat{v}}{R_{load}}$$

$$P_{C-out} = P_{0-steady} + \frac{2V_0\hat{v}}{R_{load}} \quad (5)$$

$$C(V_0 + \hat{v}) \frac{d(V_0 + \hat{v})}{dt}$$

$$V_0 \text{ constant} \rightarrow \frac{dV_0}{dt} + \frac{d\hat{v}}{dt} : 0 + \frac{d\hat{v}}{dt}$$

$$\hookrightarrow C(V_0 + \hat{v}) \frac{d\hat{v}}{dt}$$

$$= C V_0 \frac{d\hat{v}}{dt} + (\hat{v}) \frac{d\hat{v}}{dt}$$

$\hat{V} \cdot \frac{d\hat{V}}{dt} \rightarrow$ very small \rightarrow drop it
 $\hat{d}x$

$$\approx C V_0 \frac{d\hat{V}}{dt} \quad (6)$$

Put (9) (5) (6) together:

$$P_{c-in} - P_{c-out} = C V_0 \frac{d\hat{V}}{dt}$$

$$(P_{b-steady} + Gain_p \hat{A}) - (P_{\underline{0}} + \frac{\partial V_0}{R_{load}} \hat{V})$$

$$(V_0 \frac{d\hat{V}}{dt})$$

$$Gain_p \hat{A} - \frac{\partial V_0}{R_{load}} \hat{V} = (V_0 \frac{d\hat{V}}{dt})$$

Simplify div by $\frac{\partial V_0}{R_{load}}$

$$\frac{Gain_p \hat{A} R_{load}}{\partial V_0} - \hat{V} = \frac{(V_0 R_{load}) \frac{d\hat{V}}{dt}}{\partial V_0}$$

$$\frac{R_{load}}{2V_0} Gain_p \hat{I} - \hat{V} = \frac{R_{load}}{2} \frac{d\hat{V}}{dt}$$

$$\frac{R_{load}}{2} \frac{d\hat{V}}{dt} + \hat{V} = \frac{R_{load}}{2V_0} Gain_p \hat{I}$$

Define $\tau = \frac{R_{load}}{2}$

$$Gain_{DC} = \frac{R_{load}}{2V_0} Gain_p$$

$$\tau \frac{d\hat{V}}{dt} + \hat{V} = Gain_{DC} \hat{I} \quad (7)$$

Convert (7) to Laplace Domain

$$\tau \hat{V}(s) s + \hat{V}(s) = Gain_{DC} \hat{I}(s)$$

$$\hat{V}(s) [\tau s + 1] = Gain_{DC} \hat{I}(s)$$

$$\frac{\hat{V}(s)}{\hat{I}(s)} = \frac{Gain_{DC}(s)}{\tau s + 1} = Gain_{VD}(s) \quad (8)$$

Transfer function


PI Controller

Laplace Domain

$$G_C = K_P + \frac{K_I}{s}$$

$$= \frac{K_P s + K_I}{s}$$

Open loop

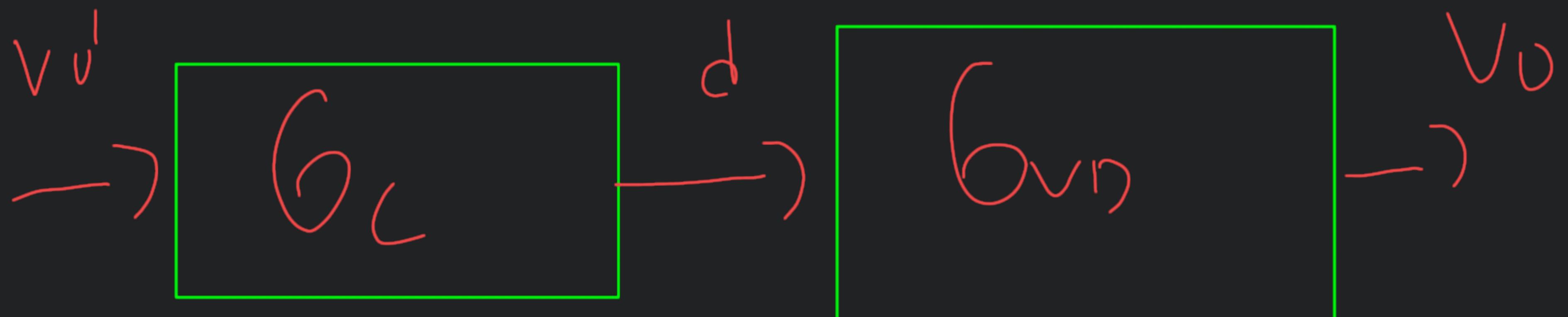

$$L(s) = G_C G_{VD}$$

$$= \frac{K_P s + K_I}{s} \times \frac{G_{DC}}{\tau s + 1}$$

$$L(s) = \frac{K_P (s + K_I / K_P)}{s} \times \frac{G_{DC}}{\tau (s + \frac{1}{\tau})} \quad (5)$$

Pole Zero Cancellation

$$G_C \rightarrow \text{Zero: } -K_I / K_P$$

